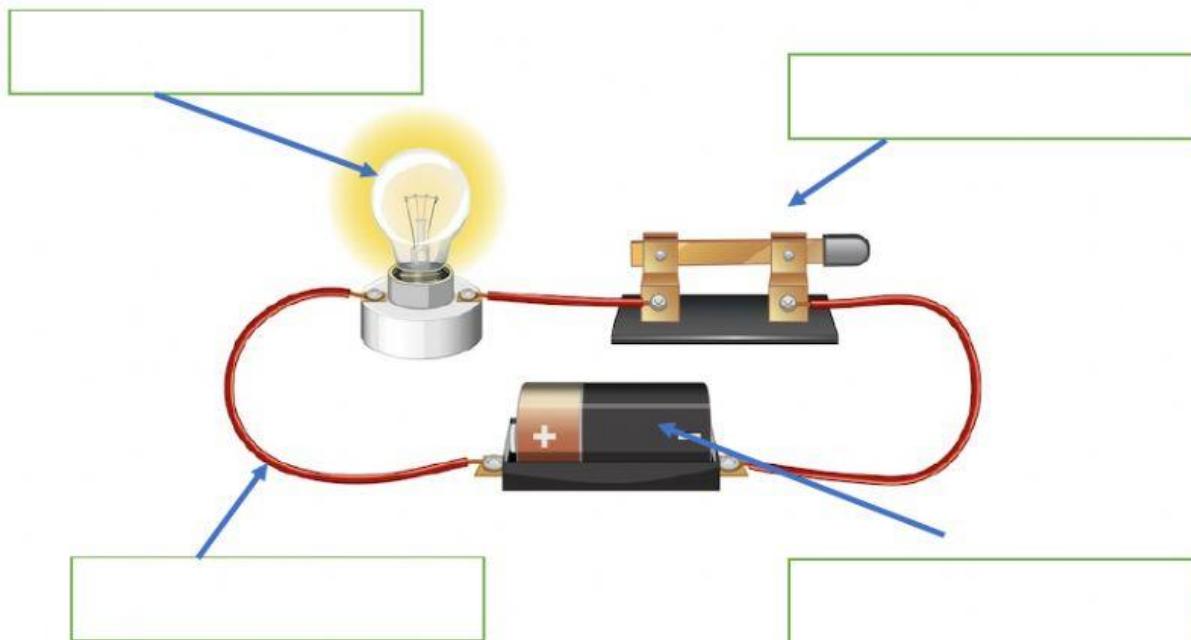


Name: \_\_\_\_\_

Date: \_\_\_\_\_

## Electric circuit

A. Name the components of the electric circuit below.



B. Describe the function of the components below.

Components	Function
Dry cell	
Switch	
Wire	

C. Answer the following questions.

1. What is the dry cell used for in the electric circuit?

2. What is the switch used for?

3. What did you observe when the switch was in the 'on' position? Why did this happen?

4. What did you observe when the switch was in the 'off' position? Why did this happen?