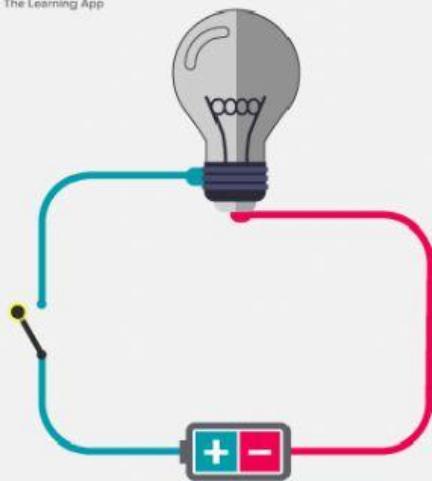


Name: _____


Date: _____

Electric circuit

BYJU'S
The Learning App



Circuit A

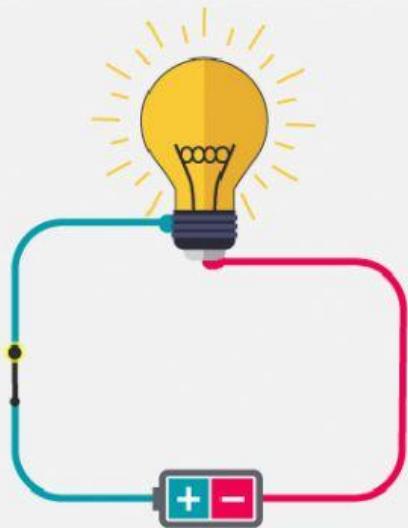

Circuit B

1. Which of the circuit above is a complete circuit?

2. What do you think will happen if the circuit is complete? Give reason.