

Name: _____

Date: _____

Electric circuit

A. Write down the names of the components below.


1.



2.



3.

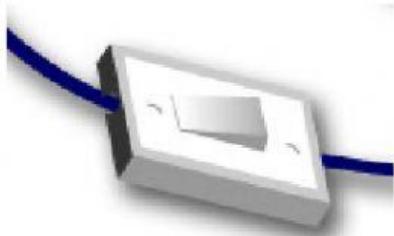

4.



B. Choose the correct answer.

negative	closes	incomplete	not light up
switch	light up	positive	path
complete	opens	source	controls

1. Electric circuit is the _____ along which electricity flow.
2. Dry cell is a _____ of electricity.
3. We can add a _____ in an electric circuit.
4. A switch _____ the flow of electricity. It _____ or _____ the circuit.
5. If the switch is 'on', the bulb will _____ because the circuit is _____.
6. If the switch is 'off' the bulb will _____ because the circuit is _____.
7. When a circuit is complete, electrons move from the _____ terminal to _____ terminals of dry cell.