

Name: _____

Date: _____

School: _____

Electricity



A) Choose the correct answer.

1. We can get electricity from _____

- A) batteries B) bulbs C) wires D) glass globes

☐

2. A switch is used to _____

- A) change electricity to light energy.
B) do work.
C) turn on electric current on or off.
D) change electricity into sound energy.

☐

3. A torchlight changes _____

- A) light energy to heat energy.
B) light energy into electricity.
C) electricity into light energy.
D) electricity into sound energy.

☐

4. Which of the following is **NOT** true?

- A) An open circuit does not allow electricity to pass through.
B) Electricity can do work.
C) Glass and wood are conductors of electricity.
D) Electricity can pass through water.

☐

5. Dry cells arranged in series give _____

- A) a weaker current and so the bulb becomes brighter.
- B) a stronger current and so the bulb becomes brighter.
- C) a weaker current and so the bulb becomes less bright.
- D) a stronger current and so the bulb becomes less bright.

☐

6. The battery is a _____ of electricity.

- A) voltage
- B) source
- C) current
- D) creator

☐

7. Without electricity, your _____ will still work in the house.

- A) computer
- B) doorbell
- C) television
- D) gas cooker

☐

8. The casing of an electric plug is usually made of _____

- A) metal
- B) plastic
- C) rubber
- D) plasticine

☐

9. Electricity cannot flow through _____

- A) water
- B) silver
- C) wood
- D) aluminium

☐

10. In an electric circuit, which parts are conductors?

- 1. filament
 - 2. wires
 - 3. glass bulb
 - 4. metal tip
- A) 1 and 2
 - B) 1, 2 and 3
 - C) 1, 2 and 4
 - D) All of the above

☐

B) Choose the correct answer.

11. The [open, closed] circuit allows electricity to pass through it.

12. [Metal, Glass, Rubber] is a conductor of electricity.

13. Electricity comes to our home from [batteries, generators, lamp] in power stations.

14. We must not touch the switch with [dry, wet, warm] hands because water is a good conductor of electricity.

15. A [bulb, switch, wire] is used to cut off an electric current in a circuit.

C) Choose True or False.

16. Batteries cannot store electricity.	True	False
17. Electricity is a form of energy.	True	False
18. The brightness of the bulb depends on its voltage.	True	False
19. When a bulb fuses, it can be reused again after sometimes.	True	False
20. Electrical energy can be converted into heat energy.	True	False