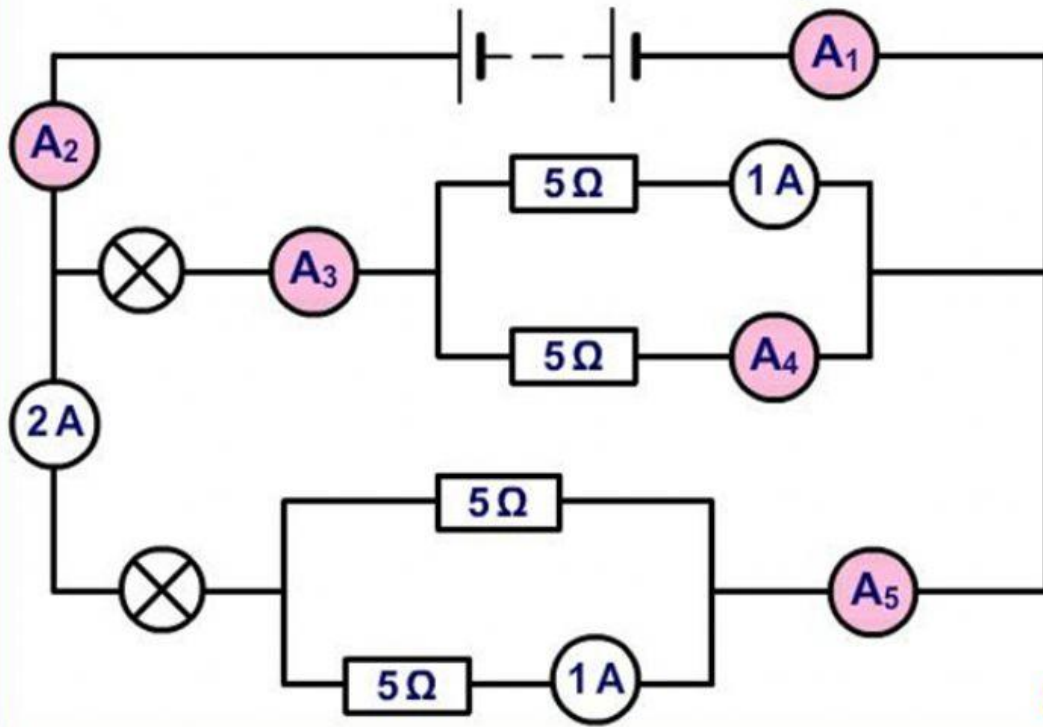


Use Kirchhoff's first law to complete the ammeter readings



ammeter
readings

8 A

4 A

3 A

2 A

1 A

$\frac{1}{2}\text{ A}$