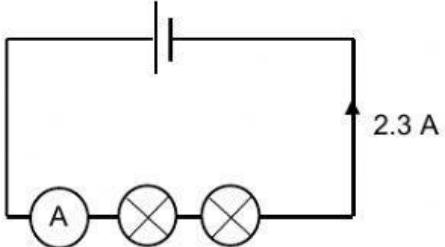
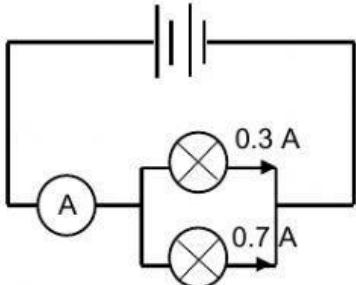
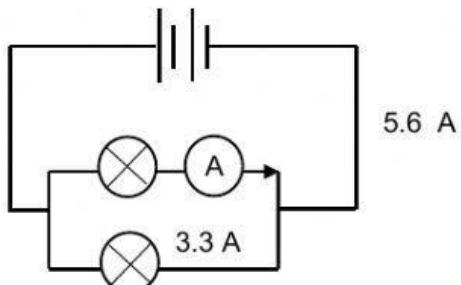
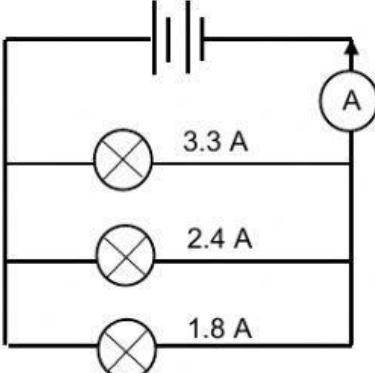
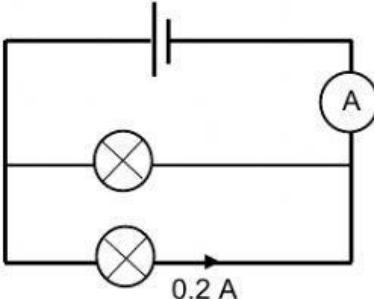


Name: ..... ( ) Class: ..... Date: .....

**LIVE Assignment 2: AMMETER READING**

	Circuit Diagram	Ammeter reading
(a)		
(b)		
(c)		

	Circuit Diagram	Ammeter reading
(d)	 <p>A parallel circuit with three light bulbs. The top bulb has a current of 3.3 A, the middle bulb has 2.4 A, and the bottom bulb has 1.8 A. An ammeter (A) is connected in series with the top branch.</p>	
(e)	<p>* please note that the two light bulbs are identical.</p>  <p>A parallel circuit with two light bulbs. The top bulb has a current of 0.2 A. An ammeter (A) is connected in series with the top branch.</p>	