

Electrical Circuits

S
T
R
E
A
M
Aid

Activity 3



You programmed a microcontroller to complete an electric circuit in unit 2.


Label the components in the microcontroller that are used to make a simple electric circuit.

Use the list provided to help.

Connector to Power source

Switch

Output light

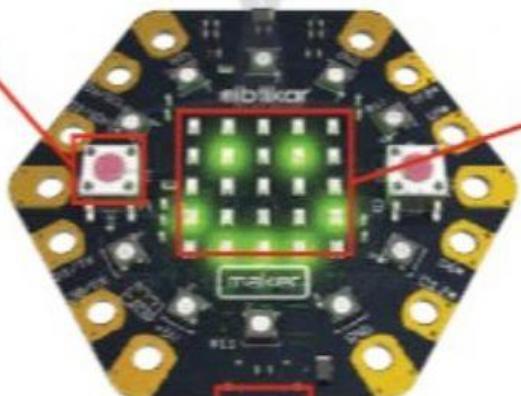

Student Feedback



48

LIVE

WORKSHEET