
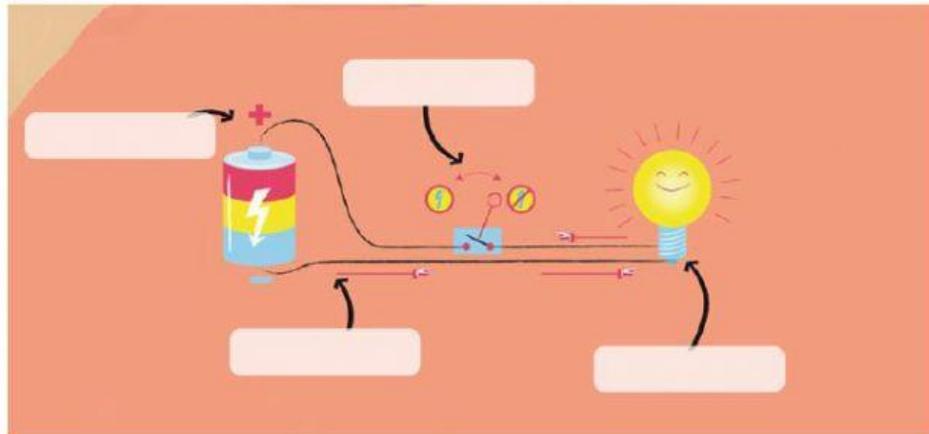


## UNIT 6. ELECTRICITY. CURRENT ELECTRICITY

### 1. Label the electrical circuit.

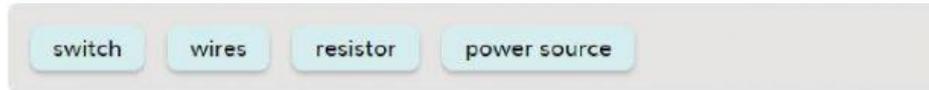

### 2. Match to make true sentences.

- |                       |   |   |   |
|-----------------------|---|---|---|
| An electrical circuit | ● | ● | allows electrons to flow through a path.                          |
| Wires                 | ● | ● | transforms electricity into other forms of energy.                |
| A resistor            | ● | ● | opens and closes the circuit and can stop the flow of electricity |
| A power source        | ● | ● | conduct electricity.  |
| A switch              | ● | ● | provides the electrical energy.                                   |