

## Parts of a circuit

Choose the name of the following images:

1. \_



2. \_



3. \_



4. \_



5. \_



6. \_



7. \_

