
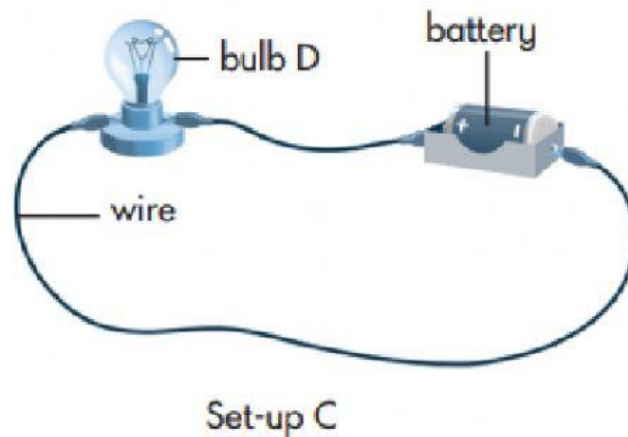
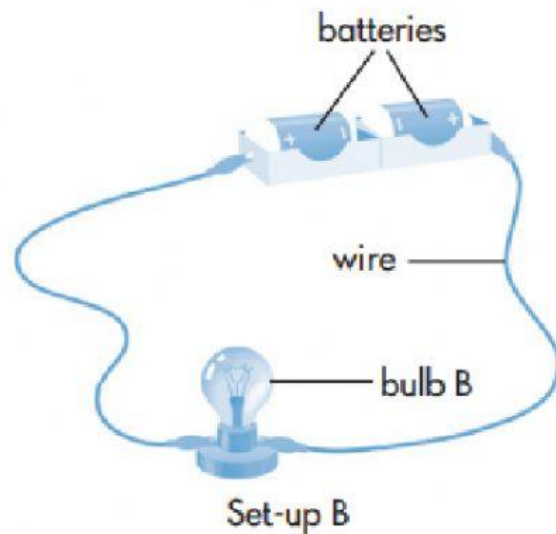


Name: _____

Date: _____

Electricity Assessment

1 Look at the set-ups.

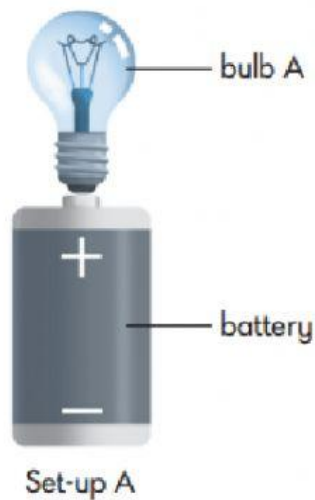

In which set up the bulb will light up? _____

Why? _____

2 Match the things into what they do in a circuit.



Battery



- Holds the battery



Wire



- Uses electricity to make sounds



Bulb



- Pushes electricity around a circuit



Buzzer



- Connects the parts of a circuit




Battery holder



- Uses electricity to give off light

3 Look at this circuit.

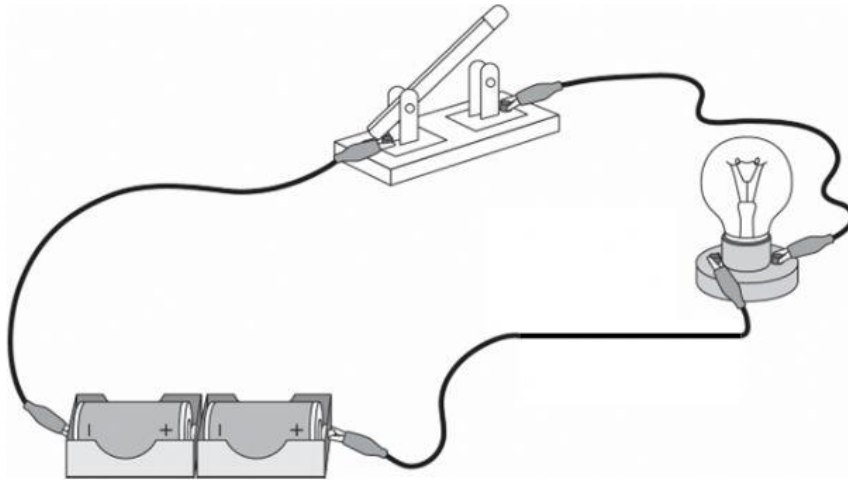

When the switch is open, the bulb will not light up, because _____

The bulb is replaced with a buzzer, what will happen when the switch is closed?

What is the switch used for?



A. I can do the worksheet by myself



B. I need a little help



C. I need a lot of help