



Name: _____

Date: _____



Circuits

Fill in the missing words

complete

energy

path

positive

loop

negative

electricity

A circuit is a _____ that allows _____ to pass through it.

Electricity always travels from the _____
to the _____.

A circuit will only work if it is _____. This means it must make a complete _____, otherwise the electrical _____ cannot flow.

Draw arrows on the diagram to show which way round the electricity is flowing.

