

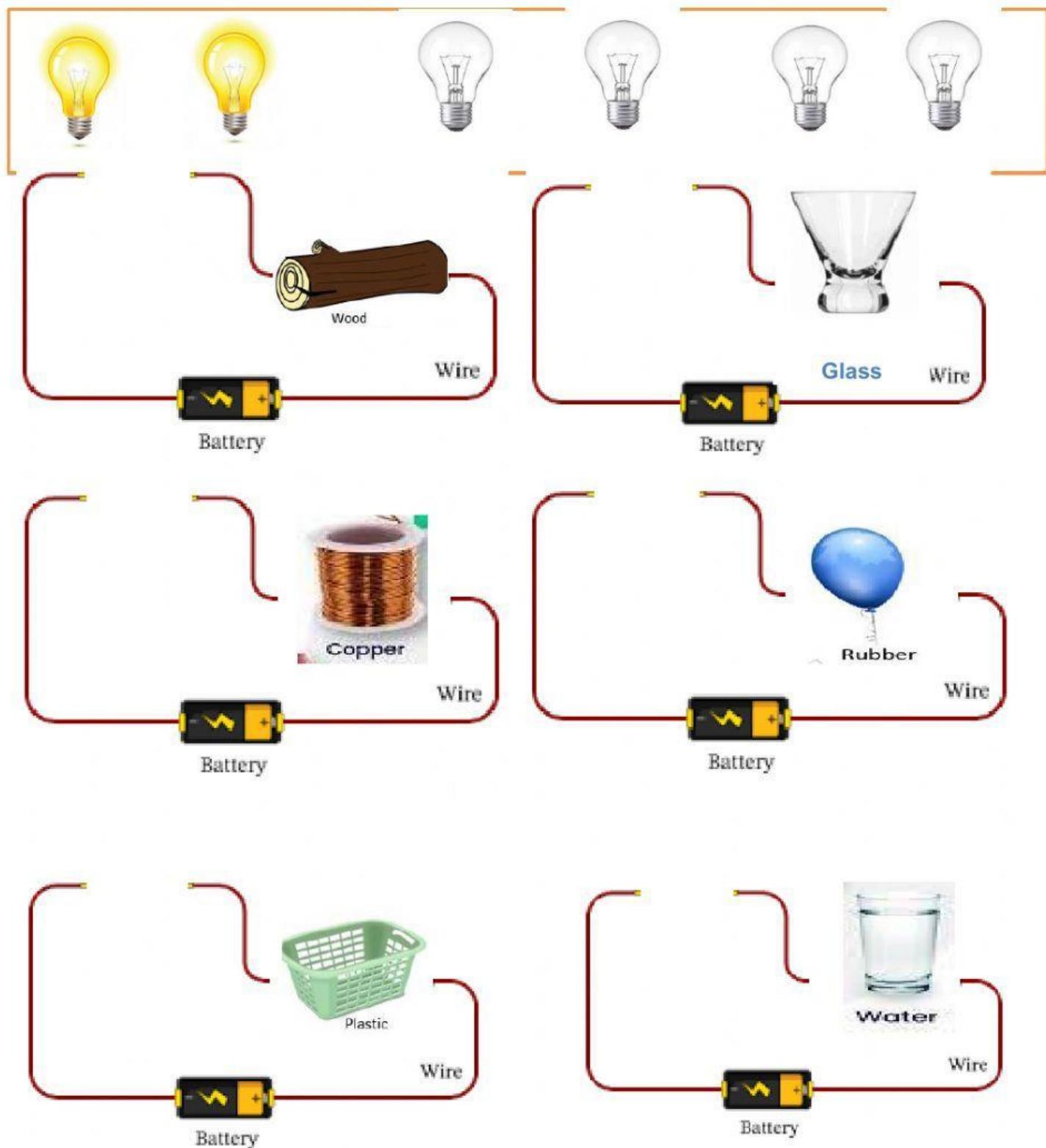
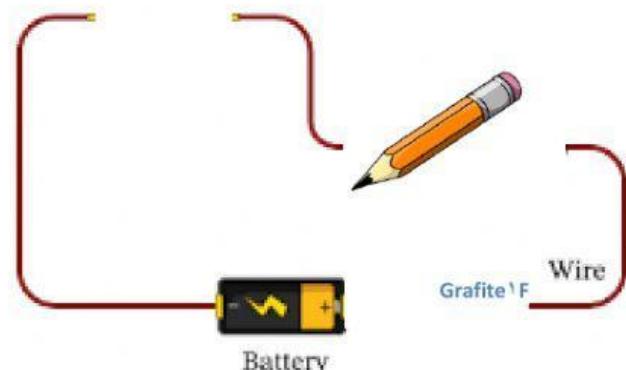
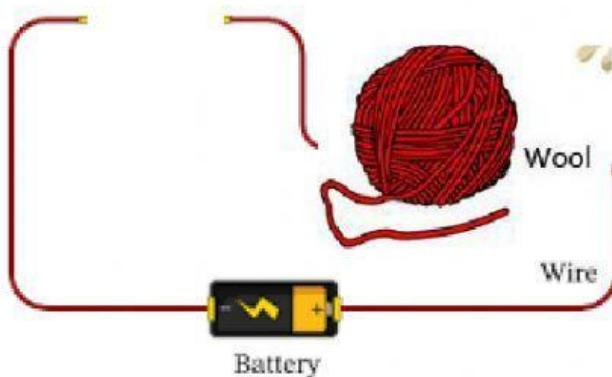


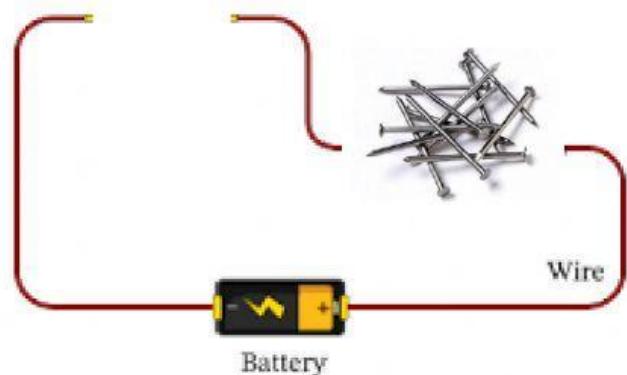Will the bulbs be on or off? Use your knowledge of electric conductor and insulators to drag and drop the suitable light bulb into the circuits below:



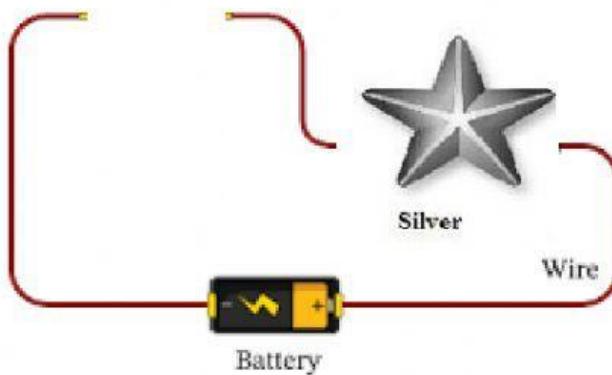

Click to show whether the material is electric conductor or insulator:

Material	Conductor	Insulator
Silver spoon		
Plastic ruler		
Aluminum foil		
Metallic key		