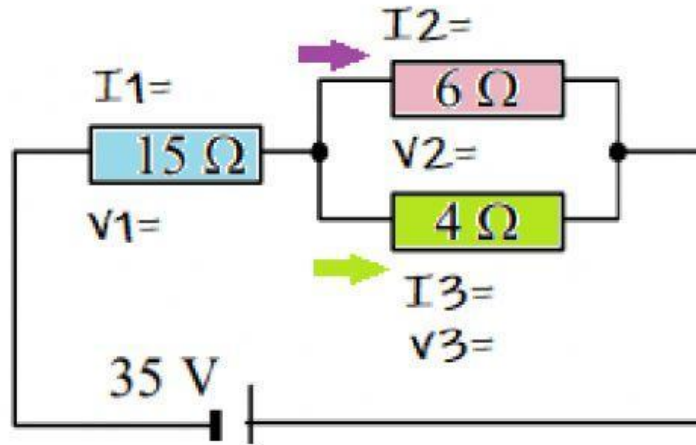


1.-Del siguiente circuito, calcula todos los valores de tensión e Intensidad



1,2 A

4,8A

35 V

2 A


2 A

30 V

4,8A

0,8A

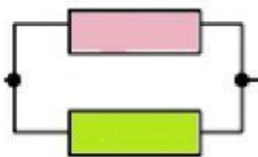2.-Indica de el circuito que precede las imágenes indicadas



$$1/R_{23} = 1/R_2 + 1/R_3$$

$$I_{23} = I_2 + I_3$$

$$V_{23} = V_2 + V_3$$

$$V_{23} = V_2 = V_3$$

$$I_{23} = I_2 = I_3$$

$$R_{23} = R_2 + R_3$$

