

## Parts of an electrical circuit

What part? Battery , bulb , wire , switch

Which part?

