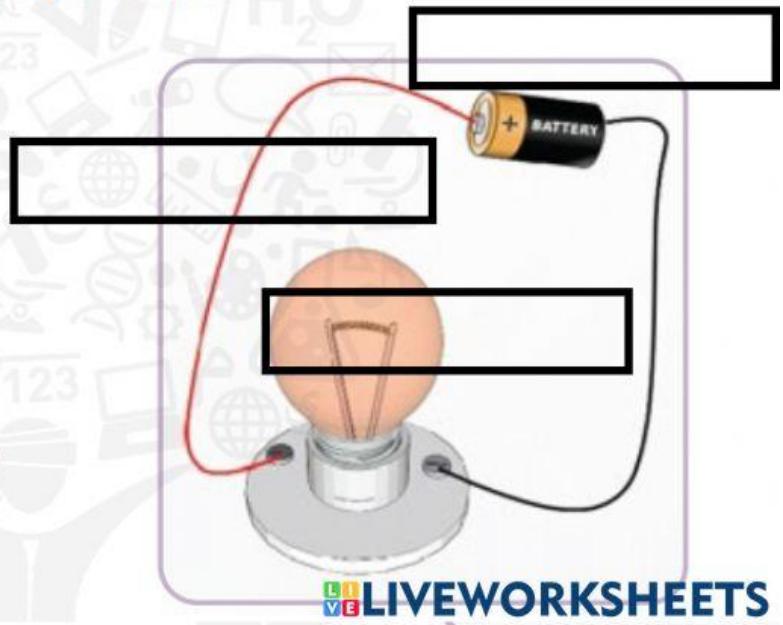




Activity 5



Look at the circuit below. Draw arrows to indicate the flow of the electric current. Start from the positive terminal of the power source.



Note that this simple circuit has:

- Ⓐ a battery - DC electrical source
- Ⓑ a light bulb – load
- Ⓒ electric wires - conductive path