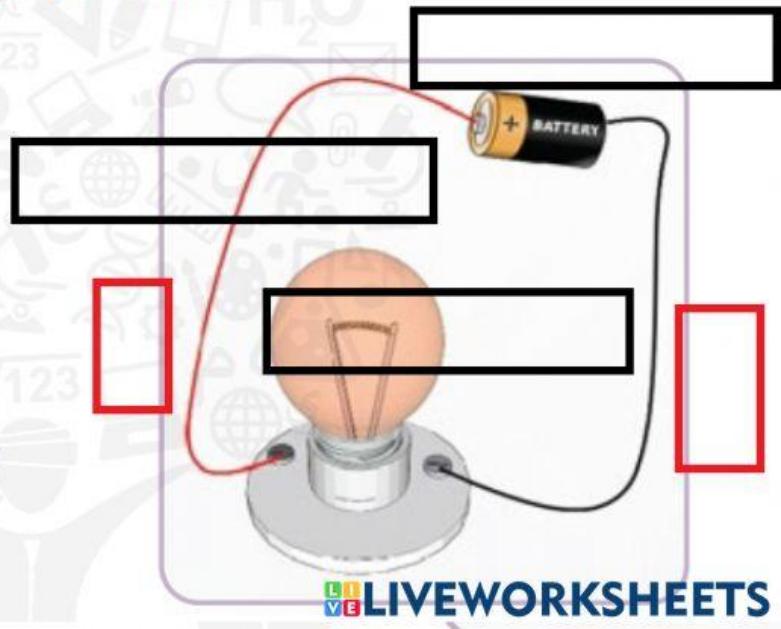




## Activity 5



Look at the circuit below. Draw arrows to indicate the flow of the electric current. Start from the positive terminal of the power source.



Note that this simple circuit has:

- Ⓐ a battery - DC electrical source
- Ⓐ a light bulb – load
- Ⓐ electric wires - conductive path

