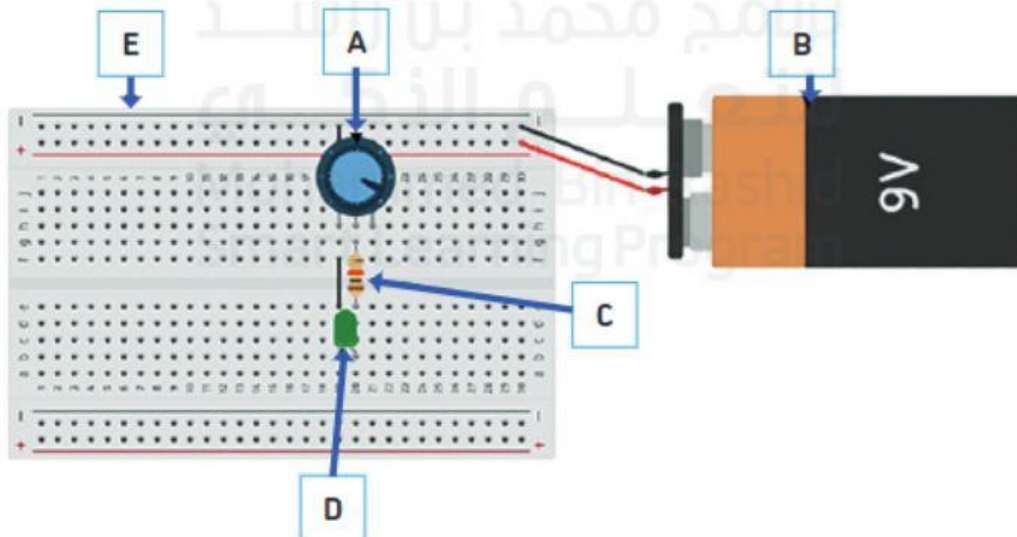


Activity 1.1.4



Study the electric circuit given below and then answer the questions below.



Breadboard

LED

Battery

Potentiometer

Resistor

Complete the table below about the given circuit diagram.

Label	Component name	Schematic symbol
A		
B		
C		
D		
E		