

Verifying Ohm's law in series and parallel circuits

Theory



Activity 8



Look at the picture below. Which LED is connected correctly? The red LED or the blue LED? Explain.

