







## Activity 12



Ahmed and Mariam are enjoying learning about **circuits**.

Help Ahmed to complete the activity that Mariam has created for him. ✓
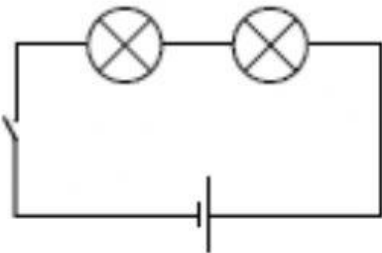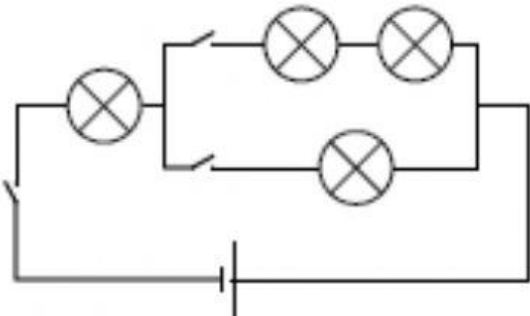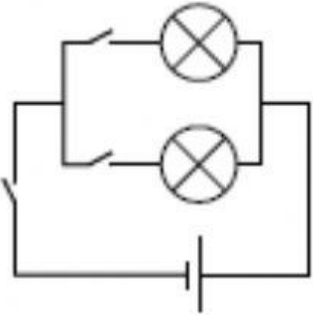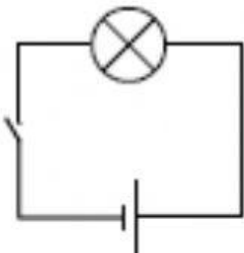
| Circuit Image                                                                       | Series circuit | Parallel circuit |
|-------------------------------------------------------------------------------------|----------------|------------------|
|    |                |                  |
|  |                |                  |
|  |                |                  |
|  |                |                  |