

Activity 10



Observe the series circuits below and complete the table by measuring the current and voltage values across each resistor using the multimeter.

Circuit diagram	Current value	Voltage value

How can you conclude that the resistors in the circuits above are connected in series? Support your answers by using Ohm's law calculations.

Smart Learning Program