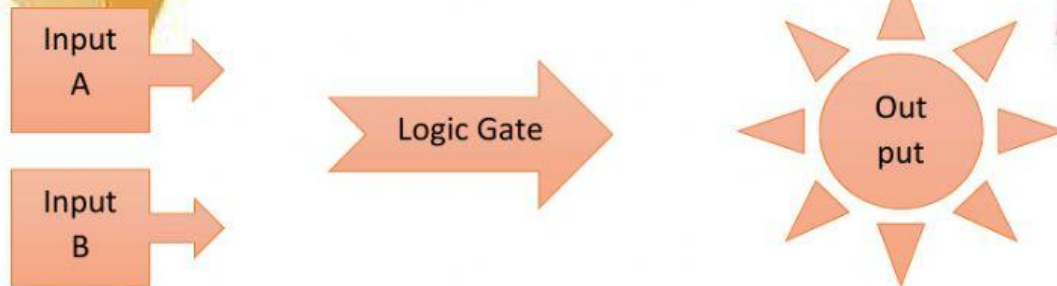


TABEL KEBENARAN GERBANG LOGIKA

Tentukan table kebenaran gerbang logika dari rangkaian berikut ini!



Gerbang logika OR

A	B	X
0	0	
0	1	
1	0	
1	1	

Gerbang logika NAND

A	B	X
0	0	
0	1	
1	0	
1	1	

Gerbang logika AND

A	B	X
0	0	
0	1	
1	0	
1	1	

Gerbang logika XOR

A	B	X
0	0	
0	1	
1	0	
1	1	

Gerbang logika NOR

A	B	X
0	0	
0	1	
1	0	
1	1	

Gerbang logika XNOR

A	B	X
0	0	
0	1	
1	0	
1	1	