

**WORKS. 4** Series and parallel circuits. Calculating the main quantities

12.01.2020

**Remember :**


When connecting receptors in a circuit, there are three possibilities, connecting them in series, in parallel or combining both ways in the same circuit (combined or mixed circuits)

Series circuit

The current (I) that flows through any receptor is the same. $I_{\text{total}} = I_1 = I_2$

The voltage (V) is shared among the elements and depends on their resistance. It is calculated using the Ohm's law. $V_{\text{total}} = V_1 + V_2$

The total resistance is the sum of the resistance in each receptor. $R_{\text{total}} = R_1 + R_2$

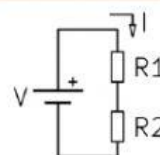**Parallel circuit**

The voltage (V) is the same in each of the receptors:


$$V_{\text{total}} = V_1 = V_2$$

The current (I) that flows through each receptor is independent.


$$I_{\text{total}} = I_1 + I_2$$

The total resistance is calculated using the equation:


$$1/R_t = 1/R_1 + 1/R_2$$

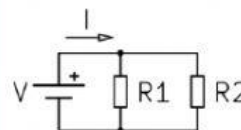**Mixed circuit**

In this case, some of the receptors are connected in series and some others in parallel. To calculate the quantities we need to make groups with the different elements according to the way they are connected and follow the steps applied for series or parallel elements in each case.

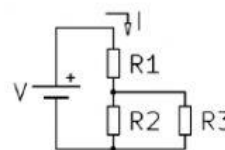**Ohm's law**

$$V = I \cdot R$$

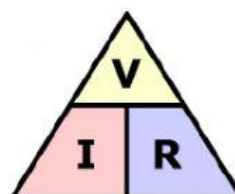


1. In the following circuit calculate:

a. Type of circuit *series/ parallel*

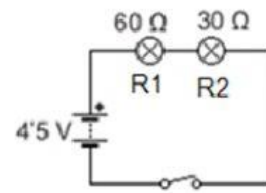b. R total:

Formula

Solution $R_{total} = \underline{\hspace{2cm}} \Omega$




2. In the following circuit calculate:

a. Type of circuit *series/ parallel*

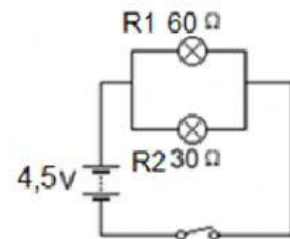b. R total:

Formula

Solution $R_{total} = \underline{\hspace{2cm}} \Omega$



3. In the following circuit calculate:

Data: $R1 = R2 = 100 \Omega$

V battery = 9 V

a. Type of circuit *series/ parallel*

b. R total: $\underline{\hspace{2cm}} \Omega$

c. I total: Formula

$I_{total} = \underline{\hspace{2cm}} A$, as it is a very small value we can pass it to miliampers $\underline{\hspace{2cm}} mA$





d. The current that flows through each bulb:

In the $\underline{\hspace{2cm}}$ circuits the current $\underline{\hspace{2cm}}$

$I_1 =$

$I_2 =$

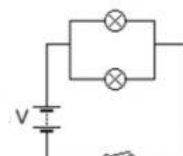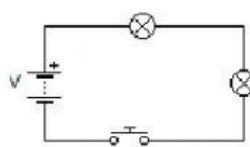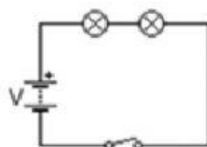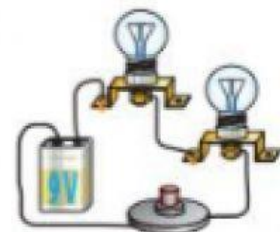e. Click on the correct diagram of the circuit that correspond to de picture above:



4. In the following circuit calculate:

Data: $R_1 = R_2 = 900 \, \Omega$ $V_{\text{battery}} = 4,5 \, \text{V}$

a. Type of circuit *series/parallel*

b. R total:

Formula:

$R_{\text{total}} = \underline{\hspace{2cm}} \, \Omega$

c. Total current (I_{total}):

Fórmula:

$I_{\text{total}} = \underline{\hspace{2cm}} \, \text{A} , \quad \underline{\hspace{2cm}} \, \text{mA}$

d. The current that flows through each bulb:

In a circuit the current in each branch of the circuit.

As the resistance in each element is the same value, the current through each bulb will be .

Consequently the total current is in the two branches of the circuit.

$I_1 = \underline{\hspace{2cm}} \, \text{A}$

$I_2 = \underline{\hspace{2cm}} \, \text{A}$

