

Circuit problems

Will the circuit work?

Look at the circuits below and use the options on the drop down list to select the correct answer

