


Identificar Tipos de Circuitos




Circuito Serie



Circuito Cerrado

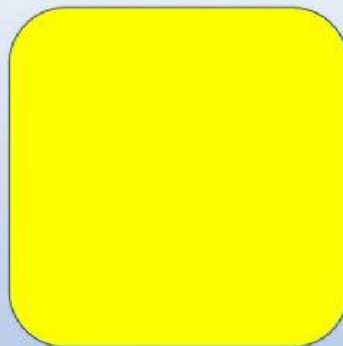

Circuito Paralelo

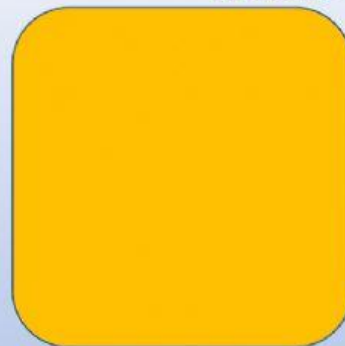

Circuito Abierto

