

**WORD BANK:**

**ENERGY – DIRECT – POSITIVE – NEGATIVE – WIRE – ELECTRICALLY -  
CONDUCTORS**

## ***Electric Current and Electric Circuits***

**Directions:** *On each line, write the term that correctly completes each sentence.*

1. The movement of \_\_\_\_\_ charged particles is an electric current.
2. Portable devices such as flashlights often use \_\_\_\_\_ current.
3. A simple circuit needs a source of \_\_\_\_\_ such as a battery.
4. A simple circuit also needs a conductor such as a(n) \_\_\_\_\_.
5. The positively charged end of a battery is called the \_\_\_\_\_ terminal.
6. The negatively charged end of a battery is called the \_\_\_\_\_ terminal.
7. Copper and aluminum make good wires in electric circuits because they are excellent \_\_\_\_\_.