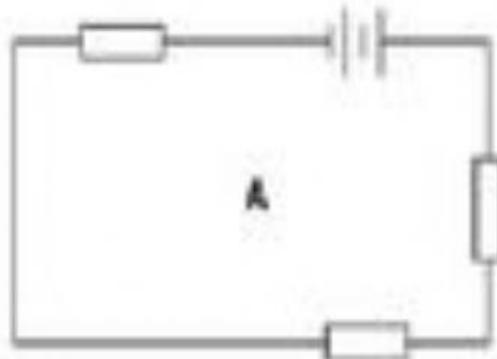


Name \_\_\_\_\_


## Series and Parallel Circuits




Identify which of these circuits are parallel circuits and which are series circuits.




A

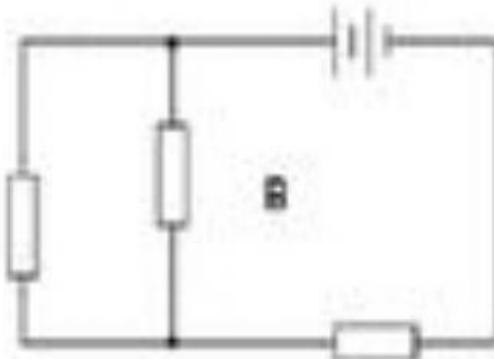


B

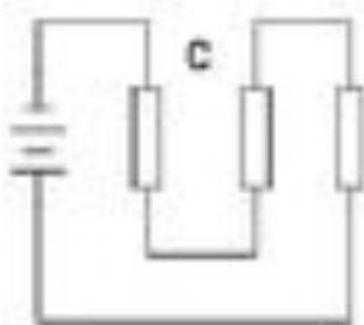


C

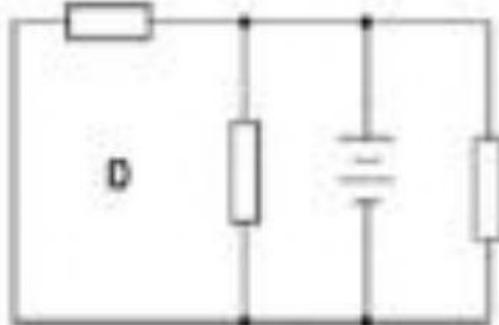

D

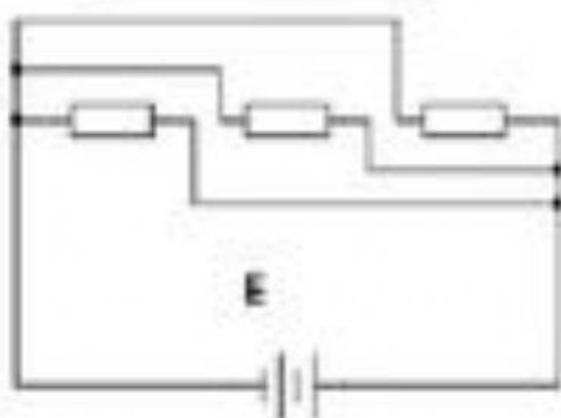

E

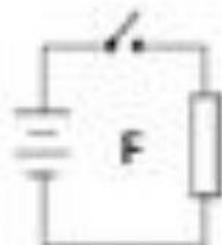

F