

Circuit or no circuit

Done by: Eng.Sara Awadalla

Define if the system given is circuit or not circuit

