


1. Label the parts of a circuit below. (4 marks)

Light bulb




Wire

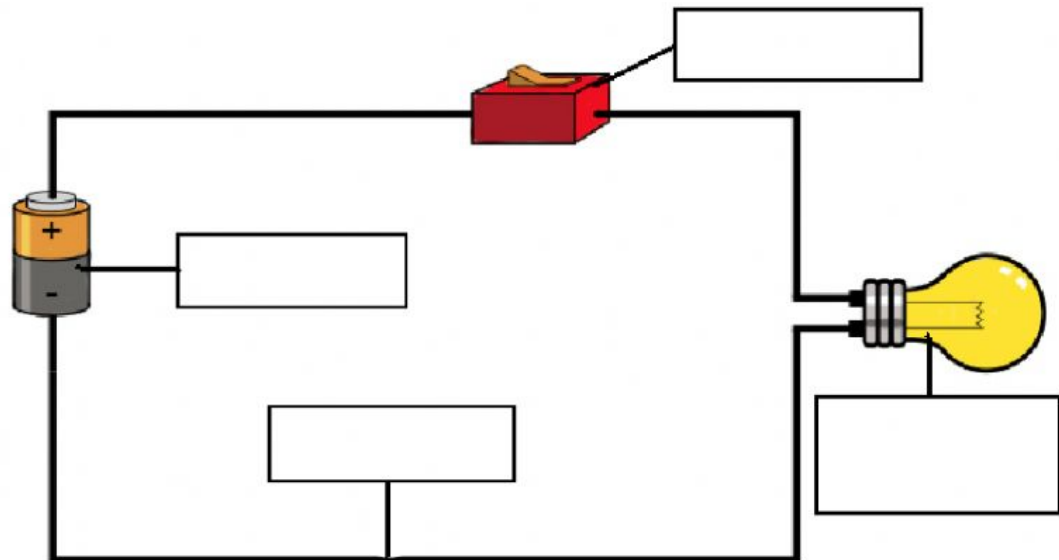


Switch

Battery



2. Name the battery-operated appliances below. (6 marks)

a) 	b) 	c) 

d) 	e) 	f) 

watch

handphone

toy car

remote

clock

torchlight