


1. Label the parts of a circuit below. (4 marks)

Light bulb



Wire

Switch

Battery

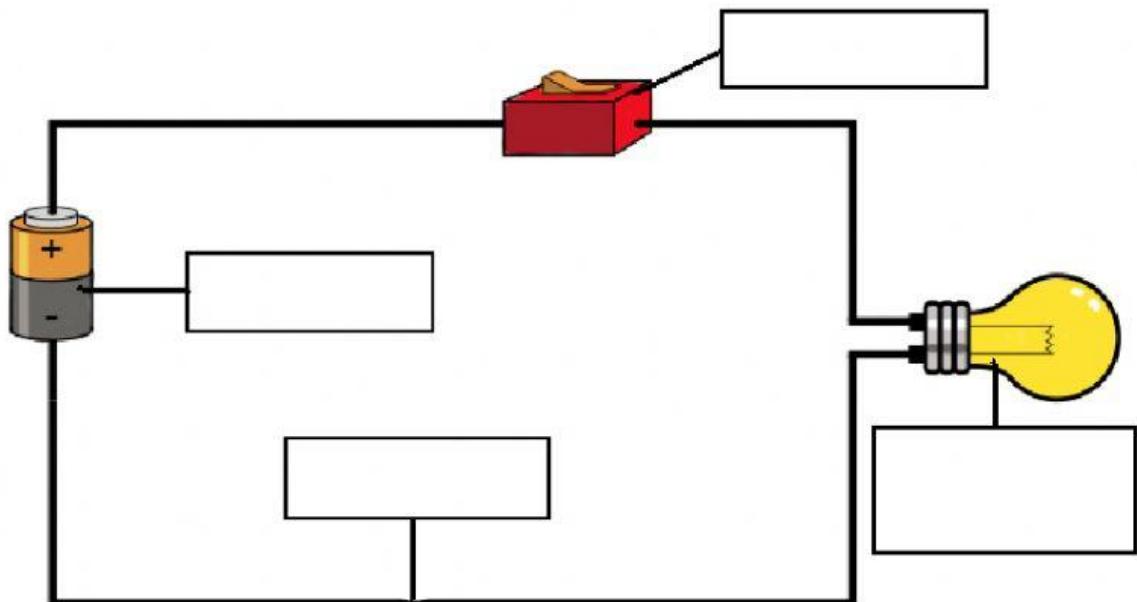

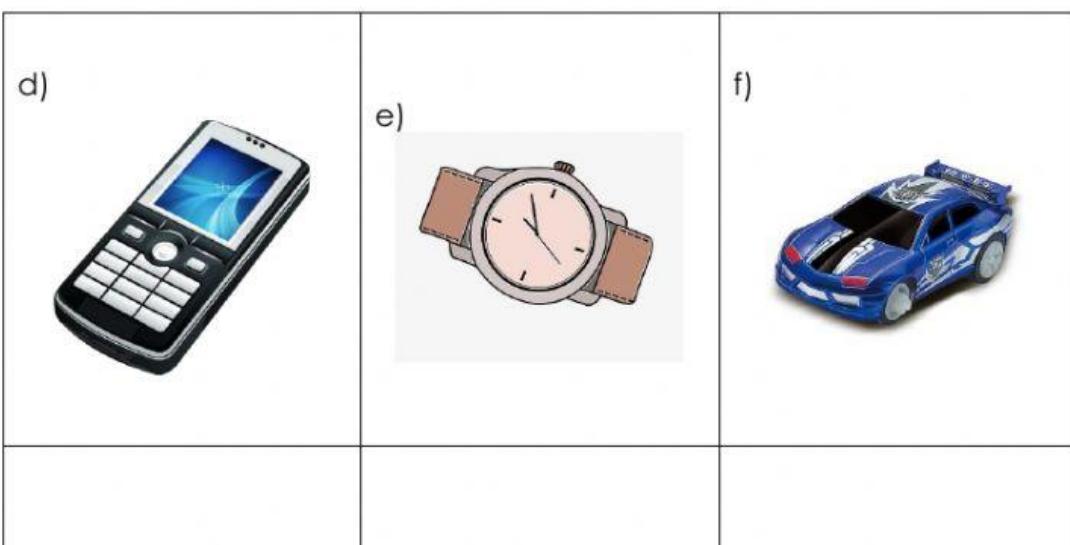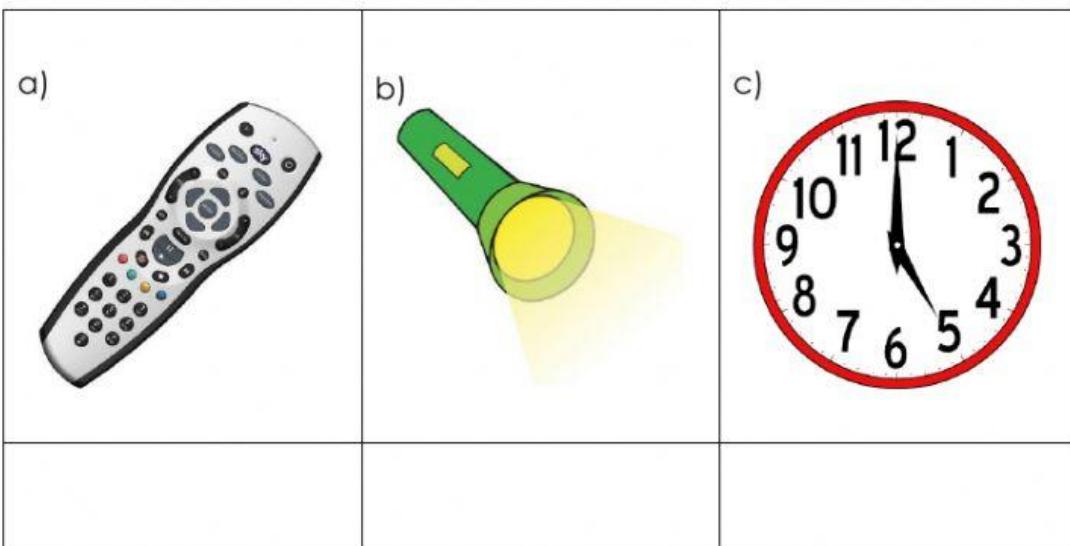2. Name the battery-operated appliances below. (6 marks)



watch

handphone

toy car

remote

clock

torchlight