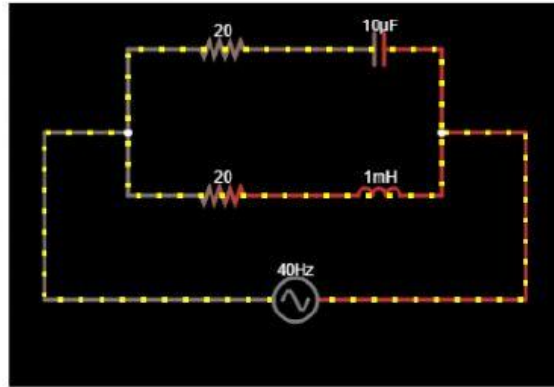


Using Complex numbers to solve RLC Circuits – M2 Worksheet



Step 1: Calculate angular velocity of this circuit:

$$\omega = 2\pi f =$$

Step 2: Calculate individual impedances for each component:

$$X_L = (\omega \times L) j =$$

$$X_C = \frac{-j}{\omega C} =$$

Step 3: Calculate the impedance in the upper branch:

$$Z_A = \text{-----} + \text{-----} j$$

Step 4: Convert Z_A to the polar form:

$$Z_A = r_1 \angle \theta_1$$

Step 5: Calculate the impedance in the lower branch:

$$Z_B = \text{-----} + \text{-----} j$$

Step 6: Convert Z_B to the polar form:

$$Z_B = r_2 \angle \theta_2$$

Step 7: Calculate the total impedance:

$$\frac{1}{Z} = \frac{1}{Z_A} + \frac{1}{Z_B} = \frac{1}{r_1} \angle -\theta_1 + \frac{1}{r_2} \angle -\theta_2 = \text{-----} + \text{-----}$$

Step 8: Write each part of $\frac{1}{Z}$ in Cartesian form that you can add them up:

Using Complex numbers to solve RLC Circuits – M2 Worksheet

Hint: convert $\frac{1}{r_1} \angle -\theta_1$ and $\frac{1}{r_2} \angle -\theta_2$ to the Cartesian form:

$$\frac{1}{r_1} \angle -\theta_1 = \text{-----} + \text{-----} j$$

$$\frac{1}{r_2} \angle -\theta_2 = \text{-----} + \text{-----} j$$

Then add them up together and find $\frac{1}{Z}$ in Cartesian:

$$\frac{1}{Z} = \text{-----} + \text{-----} j$$

Step 9: Convert the Cartesian above to polar form to flip it and find Z:

$$\frac{1}{Z} = r \angle \theta = \text{-----}$$

Step 10: invert $\frac{1}{Z}$ to get Z:


$$Z = \frac{1}{r} \angle -\theta = \text{-----}$$

Step 11: write Z in Cartesian form:


$$\text{-----} = r \cos(\theta)$$

$$\text{-----} = r \sin(\theta)$$

$$Z = \text{-----} + \text{-----} j$$

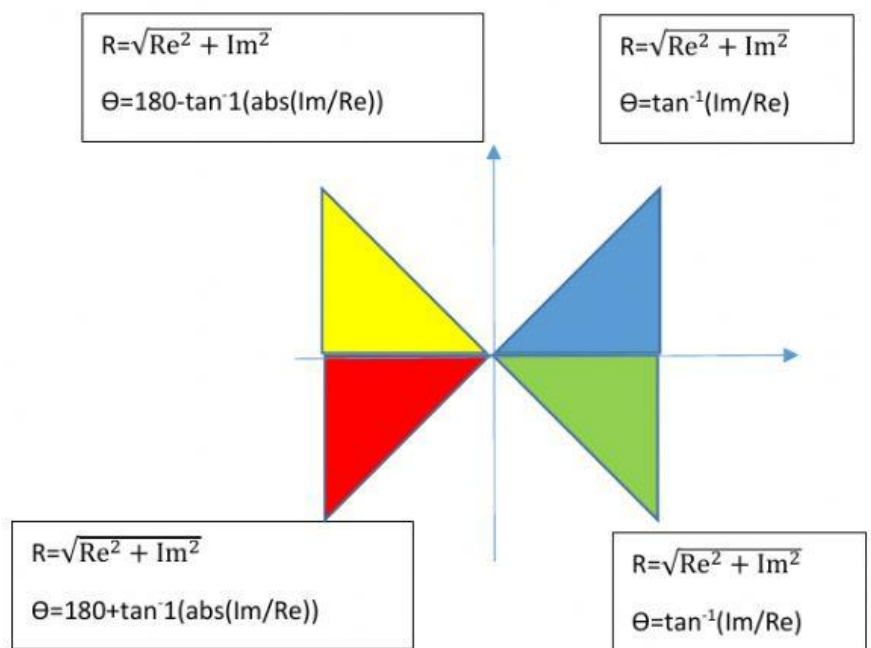

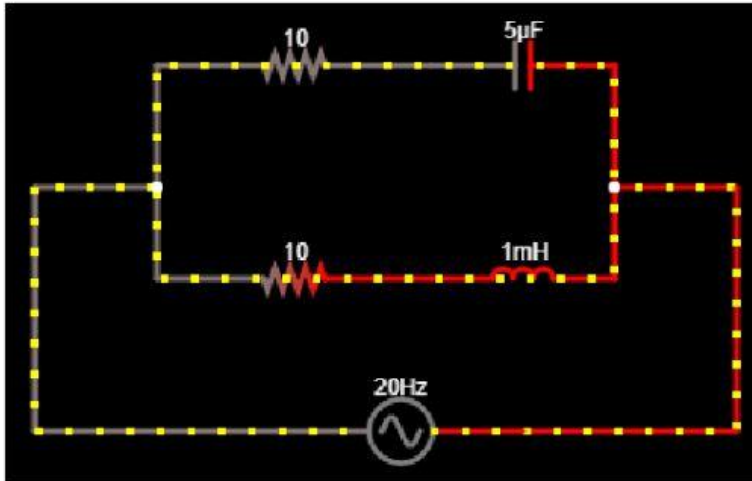Using Complex numbers to solve RLC Circuits – M2 Worksheet



Step 1: Calculate angular velocity of this circuit:

$$\omega = 2\pi f =$$

Step 2: Calculate individual impedances for each component:

$$X_L = (\omega \times L) j =$$

$$X_C = \frac{-j}{\omega C} =$$

Step 3: Calculate the impedance in the upper branch:

$$Z_A = \text{-----} + \text{-----} j$$

Step 4: Convert Z_A to the polar form:

$$Z_A = r_1 \angle \theta_1$$

Step 5: Calculate the impedance in the lower branch:

$$Z_B = \text{-----} + \text{-----} j$$

Step 6: Convert Z_B to the polar form:

$$Z_B = r_2 \angle \theta_2$$

Step 7: Calculate the total impedance:

$$\frac{1}{Z} = \frac{1}{Z_A} + \frac{1}{Z_B} = \frac{1}{r_1} \angle -\theta_1 + \frac{1}{r_2} \angle -\theta_2 = \text{-----} + \text{-----}$$

Using Complex numbers to solve RLC Circuits – M2 Worksheet

Step 8: Write each part of $\frac{1}{Z}$ in Cartesian form that you can add them up:

Hint: convert $\frac{1}{r_1} \angle -\theta_1$ and $\frac{1}{r_2} \angle -\theta_2$ to the Cartesian form:

$$\frac{1}{r_1} \angle -\theta_1 = \text{-----} + \text{-----} j$$

$$\frac{1}{r_2} \angle -\theta_2 = \text{-----} + \text{-----} j$$

Then add them up together and find $\frac{1}{Z}$ in Cartesian:

$$\frac{1}{Z} = \text{-----} + \text{-----} j$$

Step 9: Convert the Cartesian above to polar form to flip it and find Z:

$$\frac{1}{Z} = r \angle \theta = \text{-----}$$

Step 10: invert $\frac{1}{Z}$ to get Z:

$$Z = \frac{1}{r} \angle -\theta = \text{-----}$$

Step 11: write Z in Cartesian form:

$$\text{-----} = r \times \cos(\theta)$$

$$\text{-----} = r \times \sin(\theta)$$

$$Z = \text{-----} + \text{-----} j$$

$$R = \sqrt{\text{Re}^2 + \text{Im}^2}$$

$$\theta = 180 - \tan^{-1}(\text{abs}(\text{Im}/\text{Re}))$$

$$R = \sqrt{\text{Re}^2 + \text{Im}^2}$$

$$\theta = \tan^{-1}(\text{Im}/\text{Re})$$

