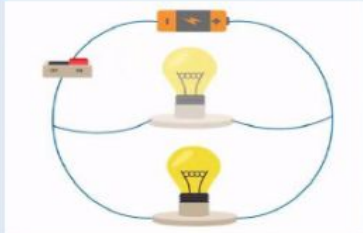


**KENDRIYA VIDYALAYA KANNUR**  
**LIVE WORKSHEET – TYPES OF CIRCUITS**

NAME:


CLASS:

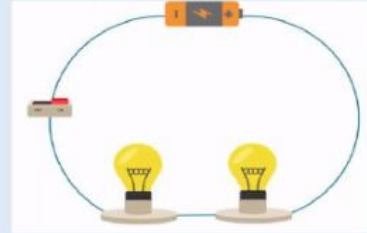**Drag & Drop**



AN EXAMPLE FOR  
SERIES CIRCUIT IS  
\_\_\_\_\_

IN A PARALLEL CIRCUIT,  
ALL THE ELECTRICAL  
COMPONENTS ARE  
CONNECTED ON AFTER  
ANOTHER IN A  
\_\_\_\_\_ LOOP



AN EXAMPLE FOR  
PARALLEL CIRCUIT IS  
\_\_\_\_\_

IN A SERIES CIRCUIT,  
ALL THE ELECTRICAL  
COMPONENTS ARE  
CONNECTED ON AFTER  
ANOTHER IN A  
\_\_\_\_\_ LOOP

DECORATION LIGHTS

SERIES CIRCUIT

TWO OR MORE

SINGLE

PARALLEL CIRCUIT

HOUSE WIRING