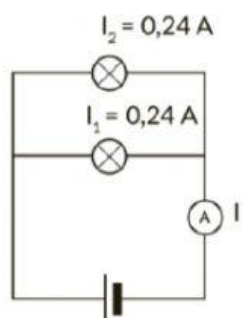



1. Tijekom vremena od 3 s kroz neki presjek žice proteče električni naboj 9 C. Električna struja kroz žicu je _____ A.

2. Nadopuni , $I =$ _____ A




3. Ampermetar A_2 pokazuje 0,22 A. Koliko pokazuje A_1 ?

A_1 pokazuje _____ A.

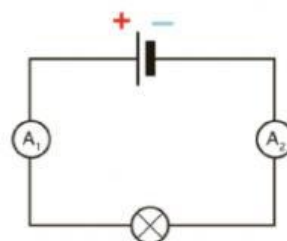


4. Što pokazuje ampermetar A?

$I =$ _____ A

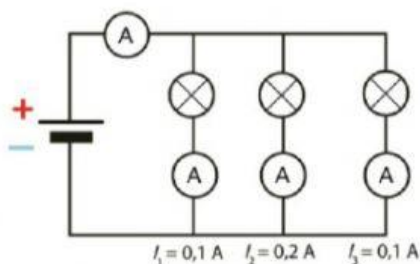


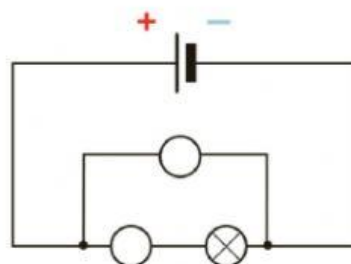5. Dopuni crtež oznakom za voltmetar i ampermetar! V i A



6. Što pokazuje voltmetar?

$U =$ _____ V

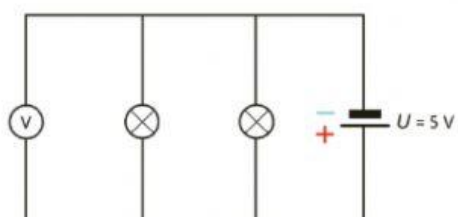

7. Baterija napona 4,5 V tijekom prolaska naboja od 1 C strujnim krugom preda trošilu energiju od _____ J.

8. Koliki je napon izvora? $U =$ _____ V

$$U_1 = 1,5 \text{ V}, U_2 = 0,5 \text{ V}, U_3 = 1 \text{ V}.$$

