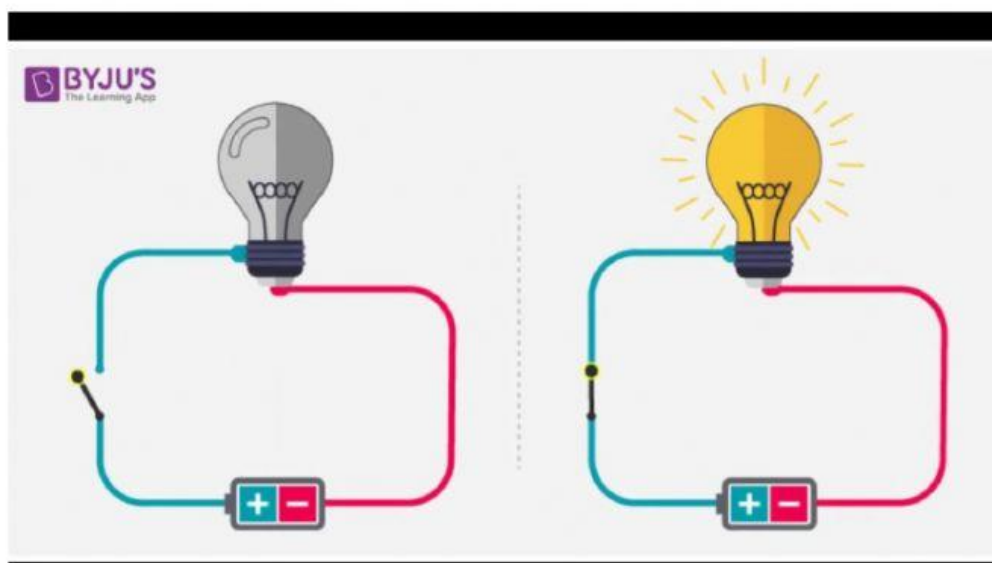



1. Cili qark elektrik eshte i hapur, cili i mbyllur?



Qark elektrik i _____

Qark elektrik i _____

2. Shkruaji elementet e qarkut elektrik

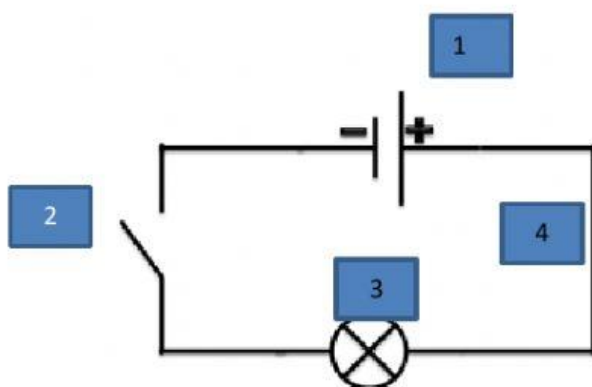

1 _____

2 _____

3 _____

4 _____