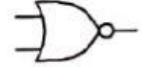


Logic gate	NAND equivalent circuit	NOR equivalent circuit
NOT		
AND		
NAND		
OR		
NOR		

Determine the truth tables for each of the logic gate circuits below. Then fit them into the right location in the table above.

