

Activity 1 (Quarter 3, Lesson 5)

Identify the terms being described in the following statements.

- _____ 1. It is the path where electric current flows.
- _____ 2. This is the source of energy in an electric current.
- _____ 3. It opens or closes the circuit.
- _____ 4. Part of the circuit that allows the electricity to flow from the source to the load.
- _____ 5. The bulbs are connected to one after another in a single chain.
- _____ 6. Each bulb is connected to the battery separately, thus, each bulb is a part of a different circuit.
- _____ 7. In this circuit, when one bulb is loosened, taken out, or busted, the other bulbs still light up.
- _____ 8. In this circuit, the more load is added, less electricity is received by each load.