

Name \_\_\_\_\_

## Lets make electric circuits

What is an electric circuit?


A ..... which allows to flow an .....  
through it, is known as .....

electric circuit

system

electric current

### Components of an electric circuit

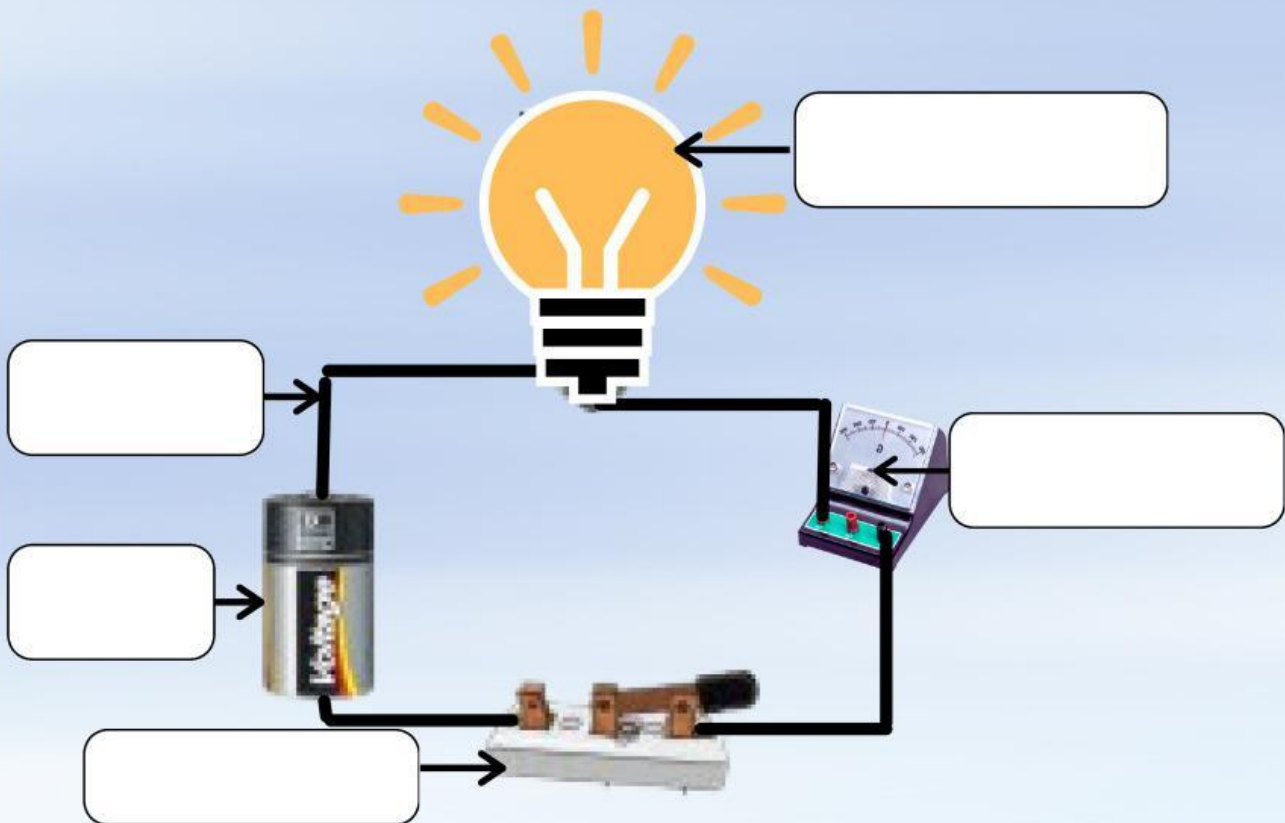

Wire


Bulb


Galvanometer

Dry cell

Switch

Drag and drop the correct symbol of each component to the correct box
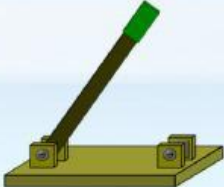
|                                                                                     |  |
|-------------------------------------------------------------------------------------|--|
|    |  |
|    |  |
|   |  |
|  |  |
|  |  |
|  |  |

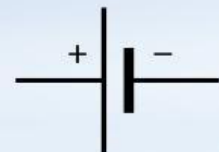

## Match the electric circuits to the correct circuit diagrams

