

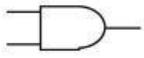



Logic Gates


Identify the following Logic Gates

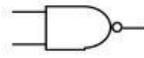


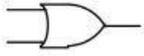



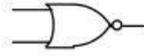

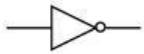

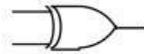

Complete the truth table for each of the following Logic Gates

0	0	
0	1	
1	0	
1	1	

0	0	
0	1	
1	0	
1	1	

0	0	
0	1	
1	0	
1	1	

0	0	
0	1	
1	0	
1	1	

0	0	
0	1	

0	0	
0	1	
1	0	
1	1	