



Activity 14



Ahmed and Mariam are learning about **open** and **short circuits**.

Help them to choose which circuits will work and which will not.

Circuit image	Will the circuit work?	
Circuit image	Yes	No