







Activity 4

Name:

Grade:

Rank these circuits below.

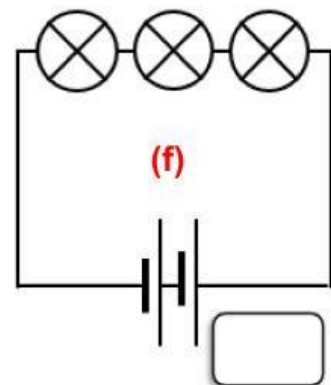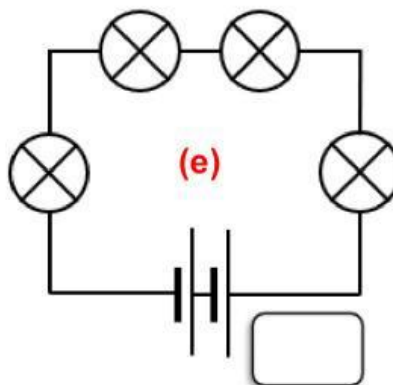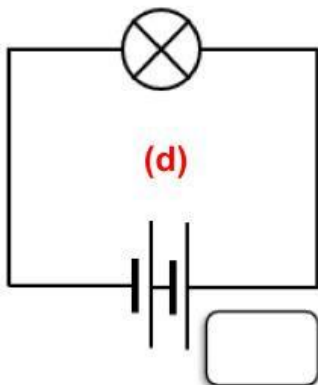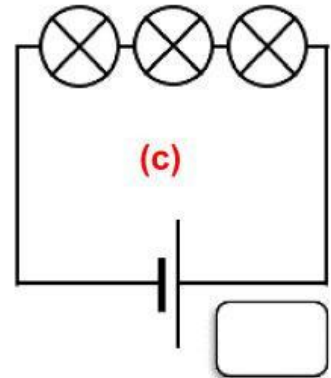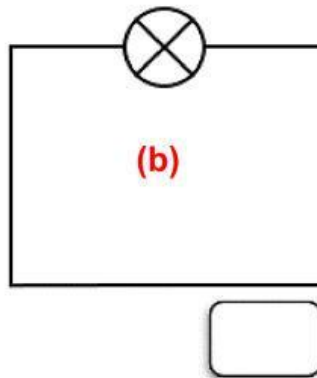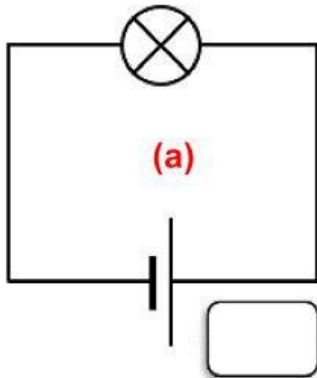Starting with the **brightest** bulb and **ending with the dimmest** bulb.



Give a reason(s) to your answer.