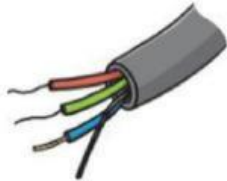
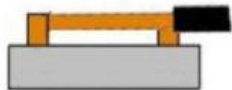
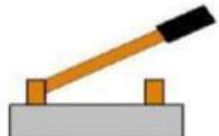
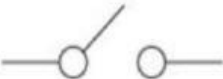


CIRCUITS

Components of a circuit and their symbols

(Thành phần một mạch điện và ký hiệu của chúng)

*components = parts

Component	Picture	Symbol	Function
			makes light using electricity
			connects components together
			turns the circuit / the light on
			turns the circuit / the light off
			gives energy or provides power

Answer these questions

CIRCUITS

1. Which component makes light using electricity?




2. Which component gives energy or provides power?

3. Which component connects other components together?

4. Which component turns the circuit / the light off?

5. Which component turns the circuit / the light on?

6. Which one is a complete circuit?

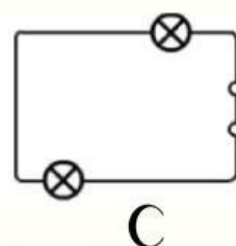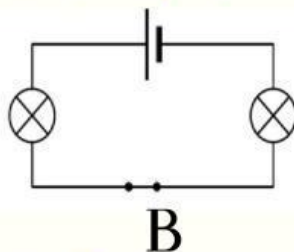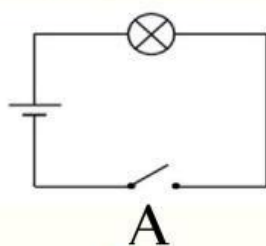

7. Which one is an incomplete circuit?

