

Fill in the blanks with the appropriate terms.

1. is a register that is used for storing logical and arithmetic data.
2. To count specific events in the computer, register are used.
3. is a bistable device that is used to construct registers.
4. Flip-flop is constructed from a set of
5. Fill the output for the below truth table (use a paper)

A	B	Output $Q = A \cdot B$	Output $Q = A + B$	Output $Q = \bar{A}$
0	1			
1	1			