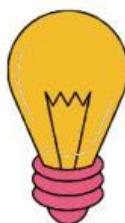



# ELECTRONIC CIRCUIT

Write the words under the pictures.

switch / battery / wire / light bulb



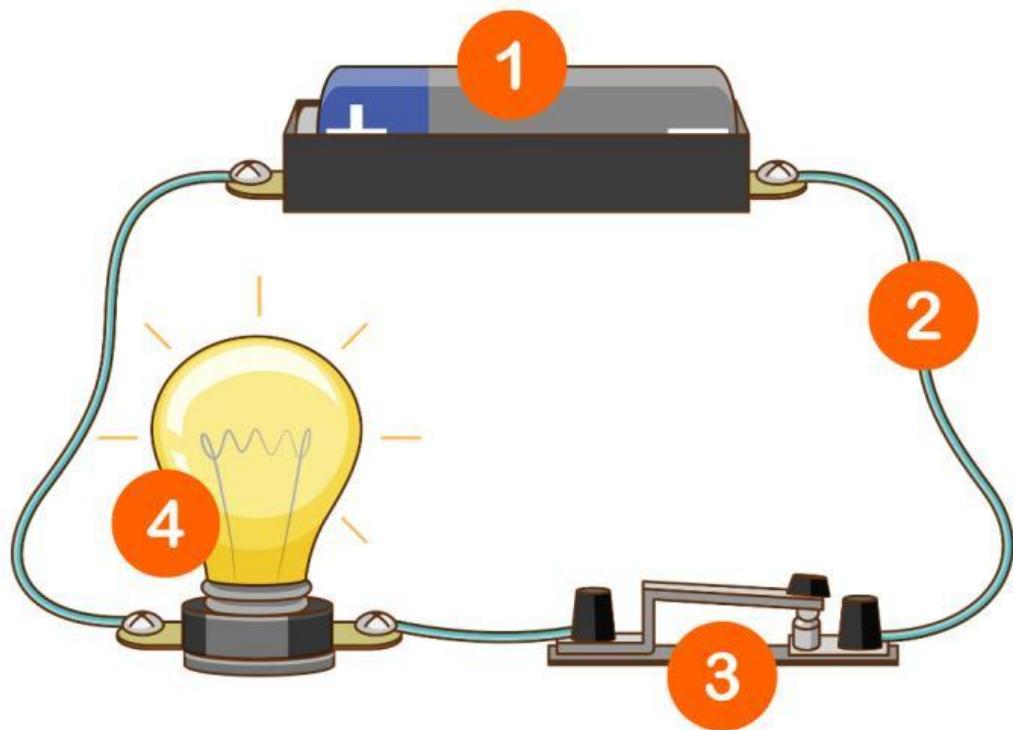Write the components of the electronic circuit below.



1- .....

2- .....

3- .....

4- .....