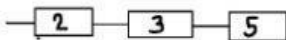
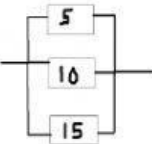
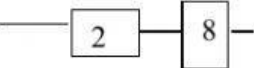
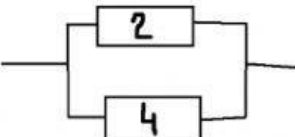


Задание 1

Сопротивление		A		Вт
Напряжение		U		Ом
Сила тока		R		В
Электрический заряд		I		Кл
		q		А

Задание 2

			
$R_{общ} =$	$R_{общ} =$	$R_{общ} =$	$R_{общ} =$
$U_{общ} = 20 \text{ В}$ $I_{общ} =$ $I(3\text{ом}) =$ $U(2\text{ом}) =$	$U_{общ} = 20 \text{ В}$ $I_{общ} =$ $I(5 \text{ ом}) =$ $U(2\text{ом}) =$	$U_{общ} = 20 \text{ В}$ $I_{общ} =$ $I(2 \text{ ом}) =$ $U(8 \text{ ом}) =$	$U_{общ} = 20 \text{ В}$ $U(2\text{ом}) =$ $I(4\text{ом}) =$