

Assume that all the switches start off closed.

Which switch if opened would turn off all the lights? A B C

