



# CONSTRUCT AND DRAW SIMPLE CIRCUIT PART 1



## OBJECTIVE OF PART 1:

Is to be able to construct different simple circuits.

## MATERIALS PART 1:

- 2 light bulbs.
- 2 batteries.
- 4 wires

## INSTRUCTIONS OF PART 1:

Using the materials In front of you try to construct a :

- circuit with one light bulb and battery.
- circuit with one light bulb and two batteries.
- circuit with two light bulbs and one battery.
- circuit with two light bulbs and batteries.

## QUESTION:

what pattern do you notice about what is required to light the light bulb?

