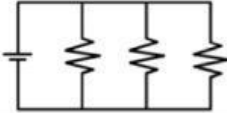
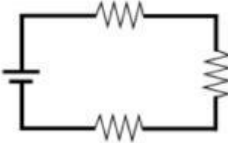


## Vocabulary Matching

Name: \_\_\_\_\_ Date: \_\_\_\_\_ Grade 4 / \_\_\_\_\_

**Objective:** Students will review key energy vocabulary by matching terms with the correct pictures.

### Match the correct image to the correct word

| Column A         | Column B                                                                             |
|------------------|--------------------------------------------------------------------------------------|
| Resistor         |    |
| Wire             |    |
| Voltage source   |  |
| Switch           |  |
| Parallel circuit |  |
| Serious circuit  |  |