

Name:		ID		Class:		Date:	
-------	--	----	--	--------	--	-------	--

ELEC 808
Class work 4 - Sum of product

Q1: From the truth table below, answer the following questions:



- Write an SOP expression for this truth table.
- Draw a gate circuit diagram corresponding to that SOP expression found in question a).

Note: A, B, C are the inputs of the circuit, Y is the output.

Truth table:

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Boolean expression 4.5 marks - each 1.5 marks
Drawing 5.5 marks

