

LEMBAR JAWABAN KAPASITOR

a. $C_{tot} =$ F

b. $Q_1 =$ C

$Q_2 =$ C

$Q_3 =$ C

$Q_4 =$ C

$Q_5 =$ C

c. $V_1 =$ V

$V_2 =$ V

$V_3 =$ V

$V_4 =$ V

$V_5 =$ V

d. $W_1 =$ J

$W_2 =$ J

$W_3 =$ J

$W_4 =$ J

$W_5 =$ J