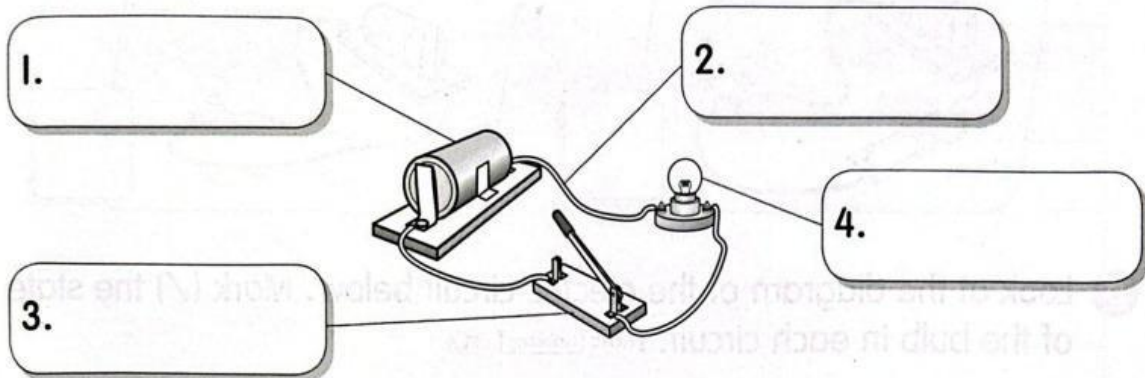


A Name the components found in the electric circuit below. **PL 1**



B Match the component of electric circuit with its function. **PL 2**

	Completes and breaks the electric circuit	
	Supplies electrical energy	
	Produces light	
	Connects the circuit with electrical components	