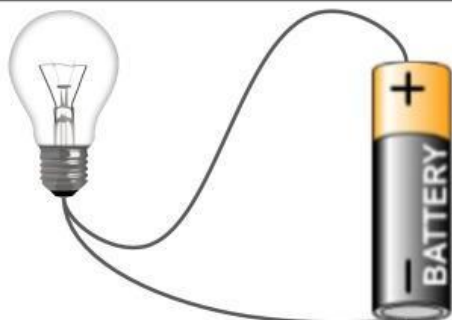


Name \_\_\_\_\_


## Electrical Circuits

For electrical current to flow, an electrical circuit needs to be a giant circle, leading from the power source, around the circuit, and back to the power source allowing electrons to flow from negative to positive.




Circle the answer  
Open Circuit or Closed Circuit

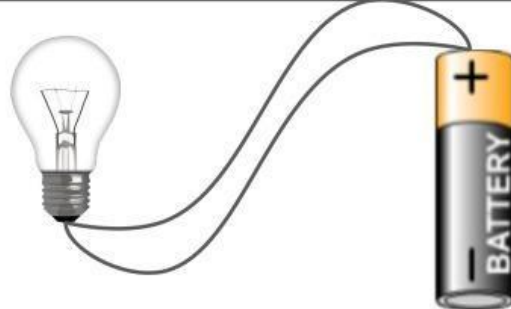Electrons can't flow or Electrons can flow




Circle the answer  
Open Circuit or Closed Circuit

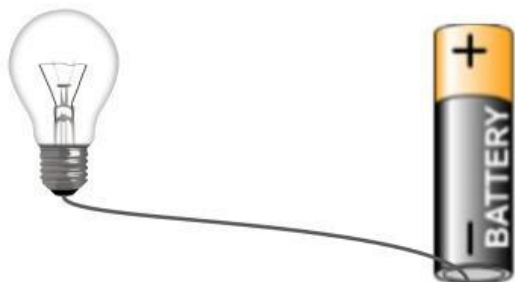Electrons can't flow or Electrons can flow




Circle the answer  
Open Circuit or Closed Circuit

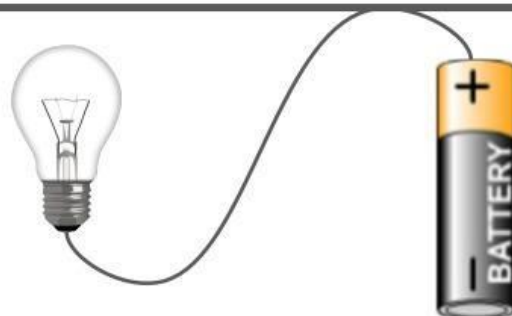Electrons can't flow or Electrons can flow




Circle the answer  
Open Circuit or Closed Circuit

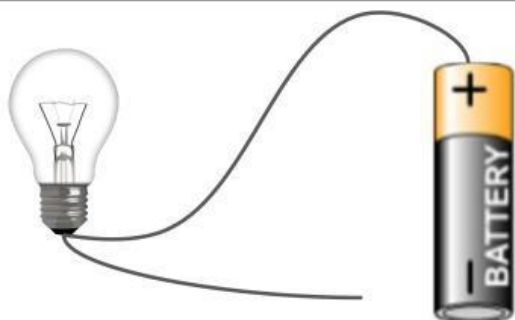Electrons can't flow or Electrons can flow



Circle the answer  
Open Circuit or Closed Circuit

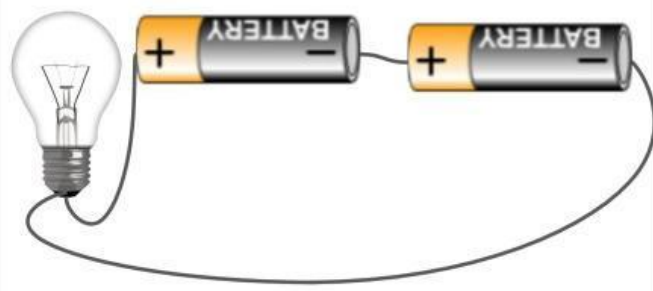Electrons can't flow or Electrons can flow



Circle the answer  
Open Circuit or Closed Circuit

Electrons can't flow or Electrons can flow